

V_oHB METHOD AND IT'S ROLE IN PA DESIGN

Timo Rahkonen

Department of Electrical and Information Engineering

Electronics Laboratory

<http://www.ee.oulu.fi/~timor>

SHORT CV

About T. Rahkonen

- Professor in “ Circuit theory and circuit design” at University of Oulu, Oulu, Finland
- PhD 1993: IC design, using CMOS delay lines for timing generation
- Research on predistortion, memory effects, EER and ET systems and switching amplifiers since 1996
- ca. 25 journal & 120 conference publications

Main publications

- J. Vuolevi et al.: Measurement Technique for Characterizing Memory Effects in RF Power Amplifiers. IEEE Trans. on MTT August 2001, pp. 1383-1389.
- J. Vuolevi, T. Rahkonen: Distortion in RF Power Amplifiers. Artech House 2003.
- J. Aikio, T. Rahkonen: Detailed Distortion Analysis Technique Based on Simulated Large-Signal Voltage and Current Spectra. IEEE Trans. on MTT October 2005

CONTENTS

1. Needs in PA design

2. Detailed distortion analysis

- Cancellation and correction of nonlinear effects
- Want to obtain more information from distortion analyses

3. Volterra-type tools

- Volterra basics
- Analysis modes and
- Visualization methods

4. Building polynomial models

- derivatives, I-V, ..
- Spectral fitting

5. Implementations of Volterra analysis

- NLSIM: matlab impl.
- VoHB: Combined fitting + Volterra on top of HB

6. What next ?

1. SIMULATION NEEDS IN PA DESIGN

Power

losses

optimum load impedance

Efficiency

disastrously low with high peak power signals (class A: 50% at FS, 9% at -10 dB)

R_{opt} , non-overlapping V & I

heavy use of exotic structures (feedforward, Doherty, predistortion, envelope tracking..)

Linearity

opposite to efficiency requirements

causes of memory effects

sweet bias points, cancellations, ...



now aiming at studying the performance of predistortion setups

Stability

large-signal system

exciting spurious oscillations without input RF signal

Pout & Efficiency vs, Zdrain

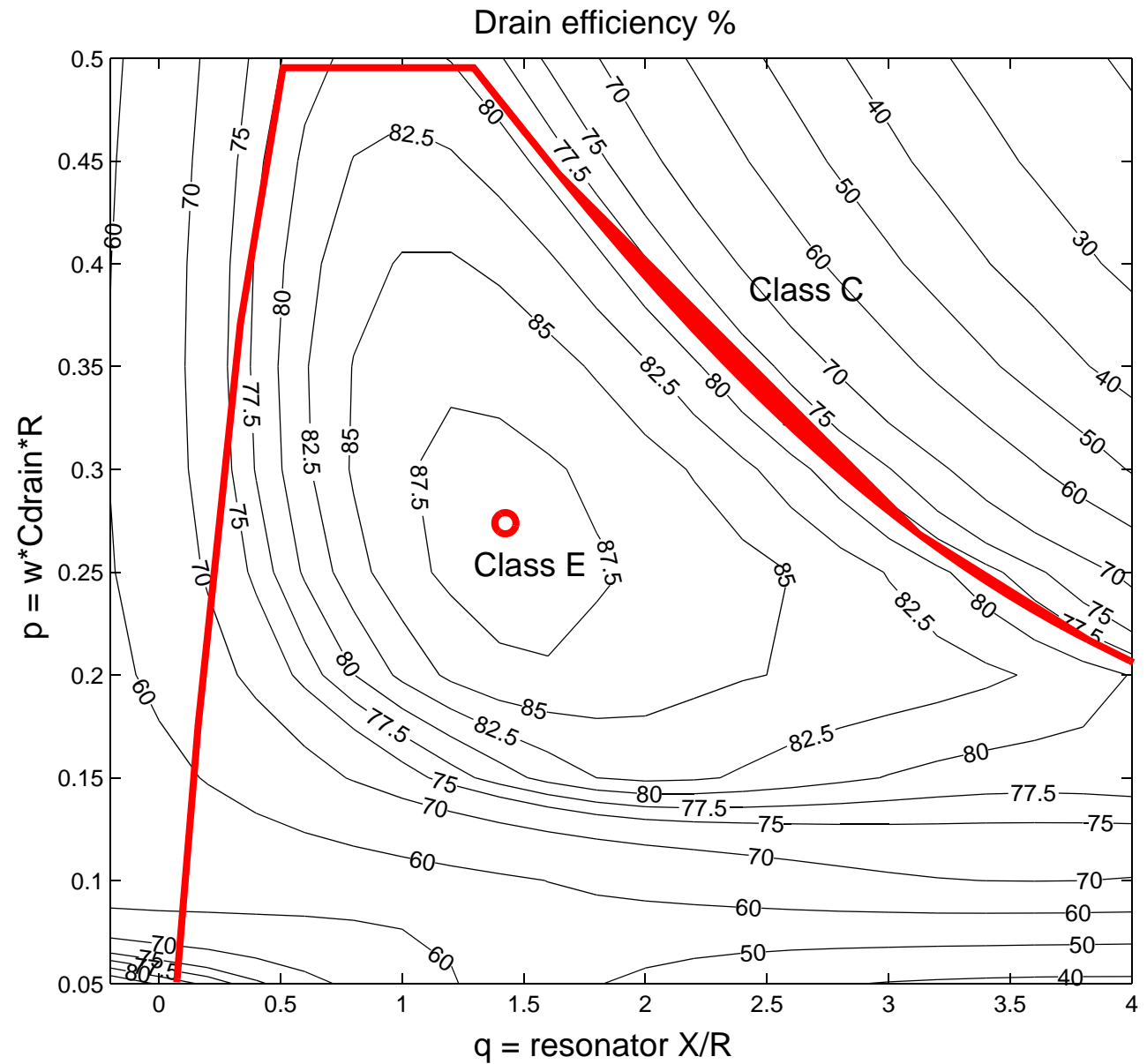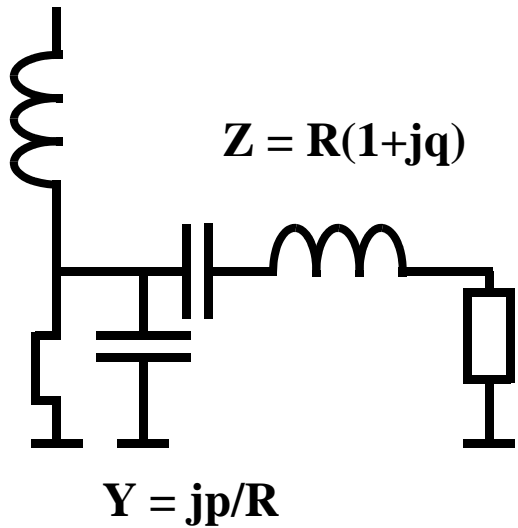

Harmonic load pull (performed by Volterra sweep)


Fundamental Z_g, Z_d fixed

Large-signal op point \sim const

Nonlinearities \sim const


**Sweeping Z_g, Z_d at BB, $2f_0$
possible using Volterra**

IM3 vs. $Z_{in}(BB)$ on Smith chart

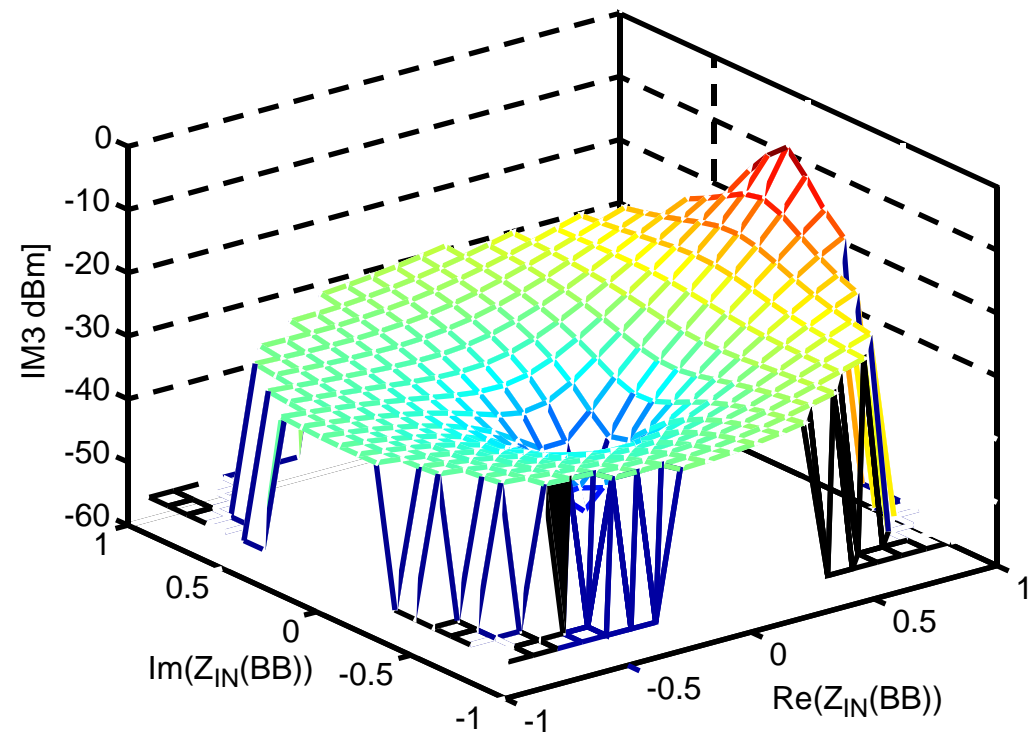


2. DETAILED DISTORTION ANALYSIS

Noise analysis

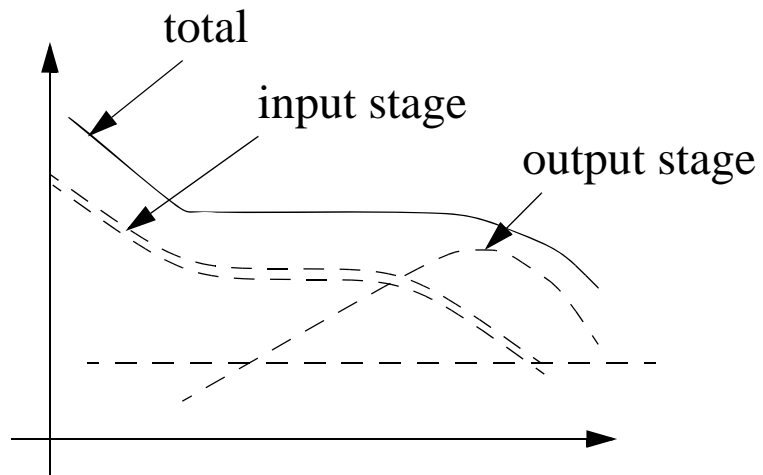

Individual contributions are shown
to see what to improve
Cheap AC analysis





Distortion analysis

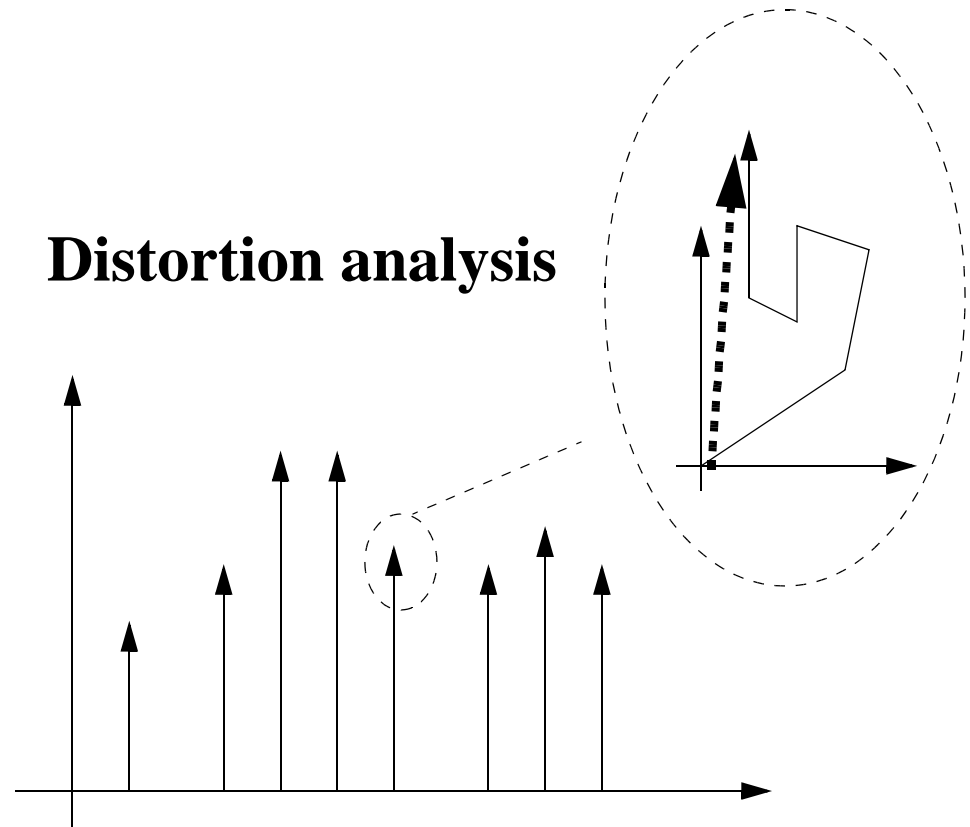

Typically, only total distortion is shown
Multitude of contributions, all having
amplitude and phase




- Memory effects
- Use of harmonic & BB shaping
for linearisation

EXAMPLE: MOS CURRENT MIRROR

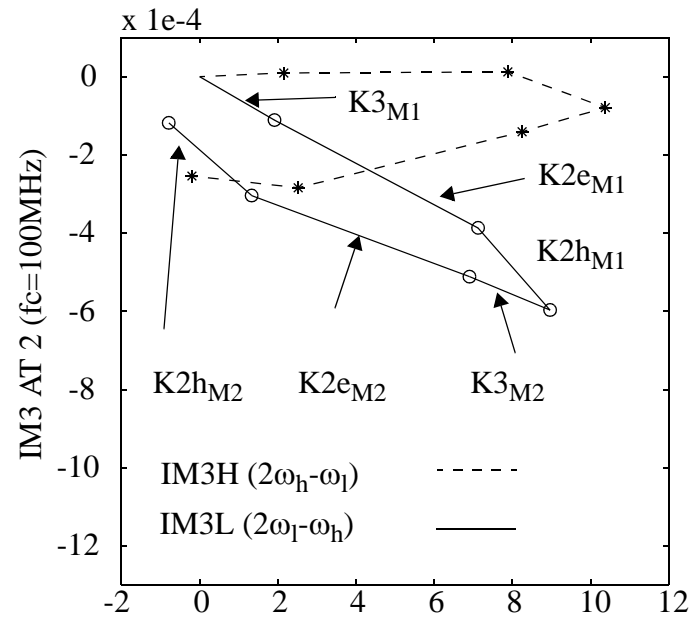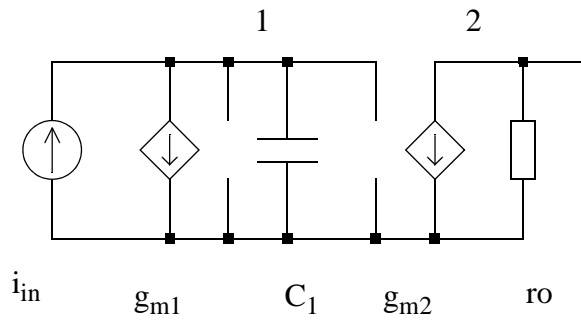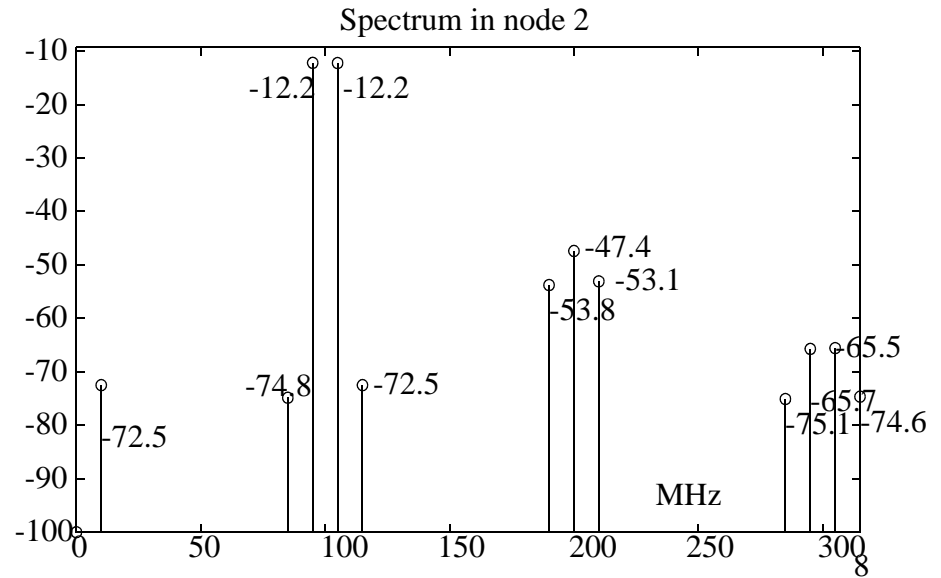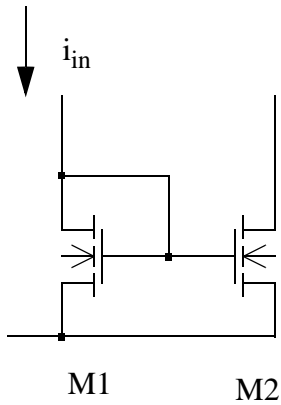

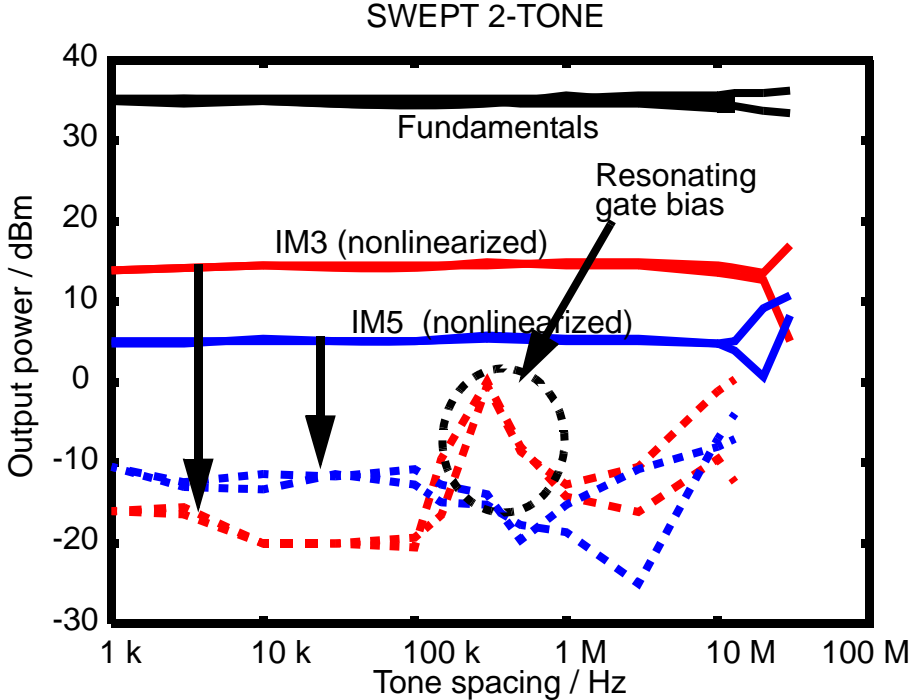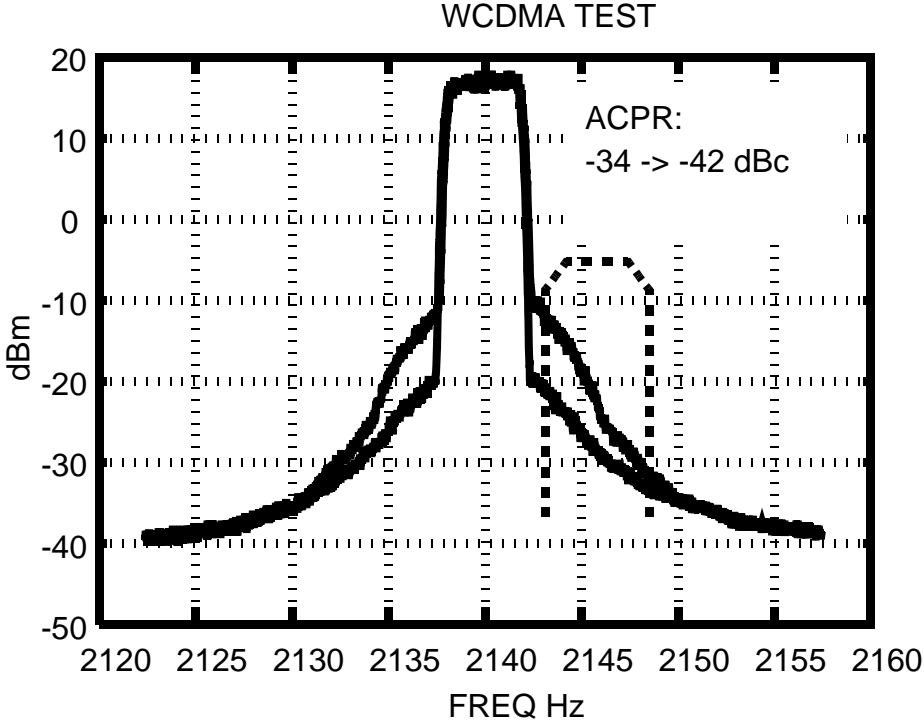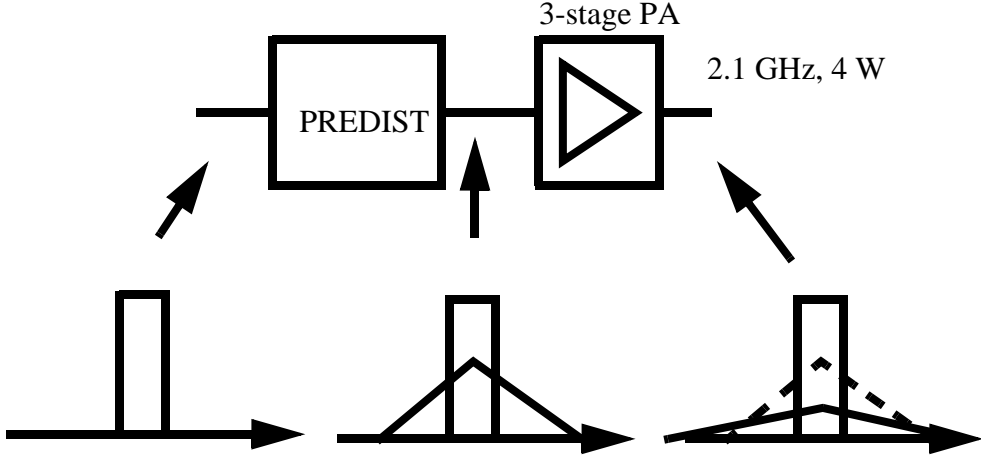
PROBLEMS IN PREDISTORTION

Achievable cancellation in predistortion depends on BW




MEMORY EFFECTS

Upconversion of BB envelope

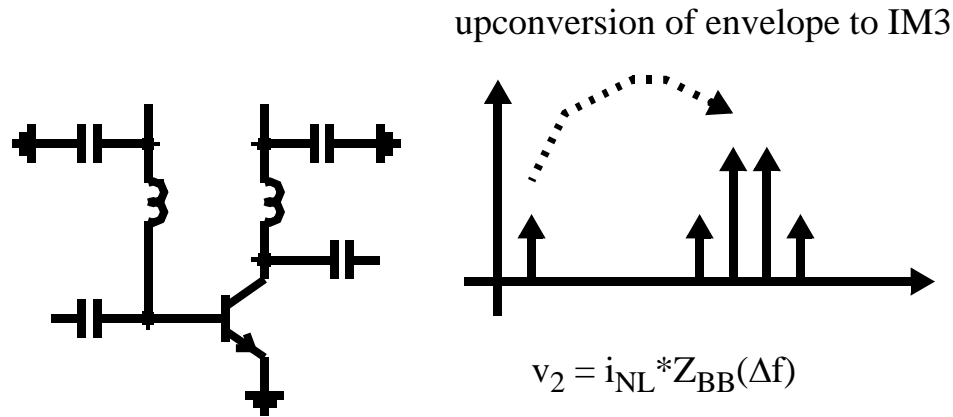


Bias shift due to envelope rectification

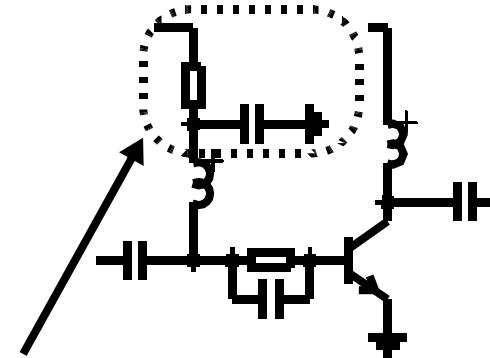


Envelope current appears as voltage and gets rectified, causing Δf dependent DC bias shift

Gain tempco + thermal feedback

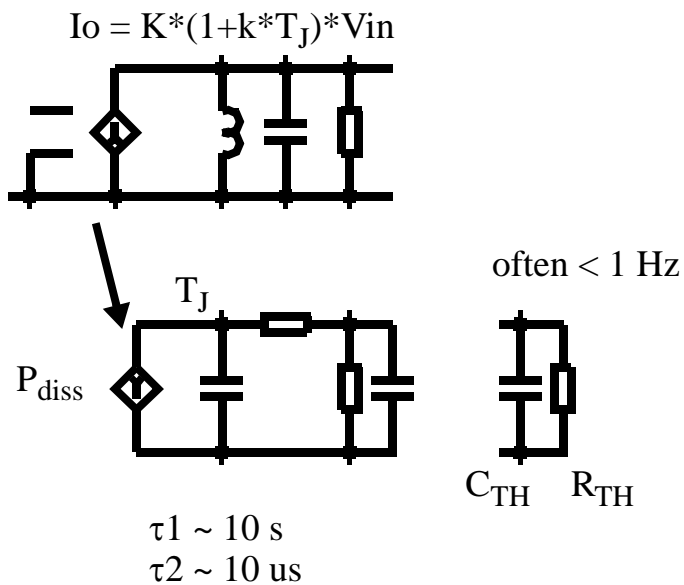





Filters between predistorter and PA

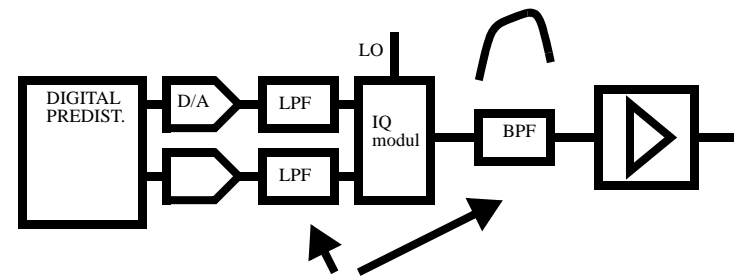

Flatness, ripple, and vector error of the filters

(Sundström)

CANCELLATION ACCURACY - MEMORY EFFECTS

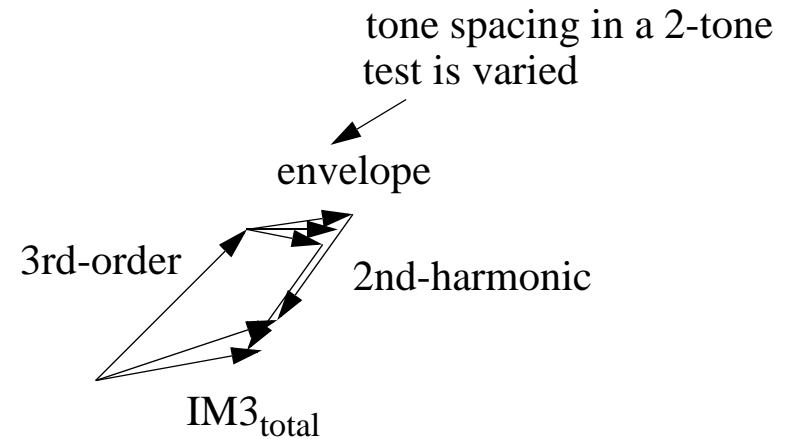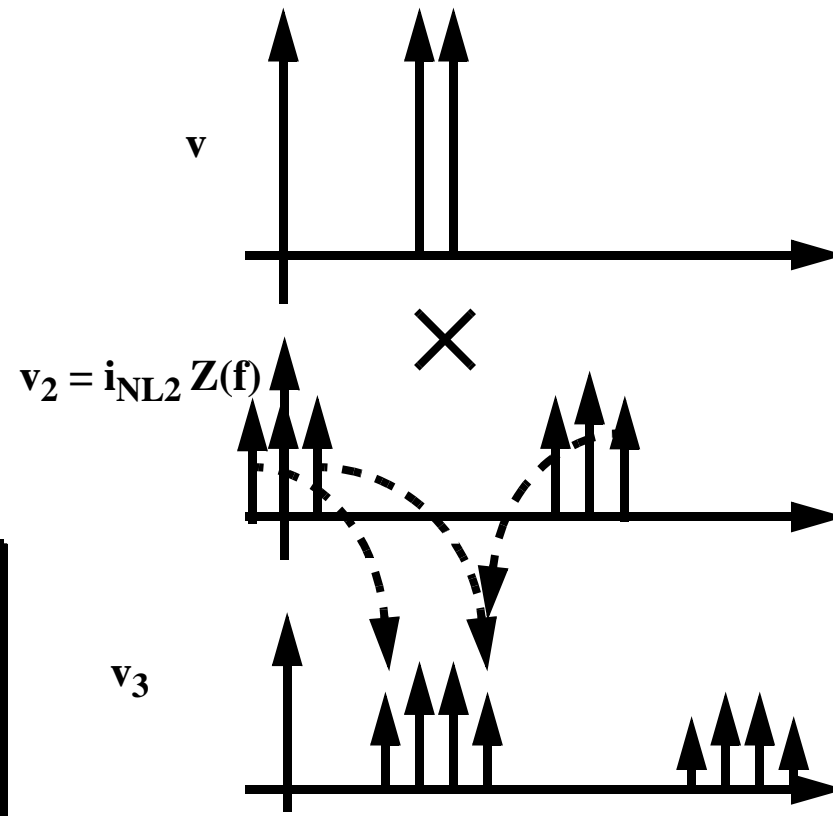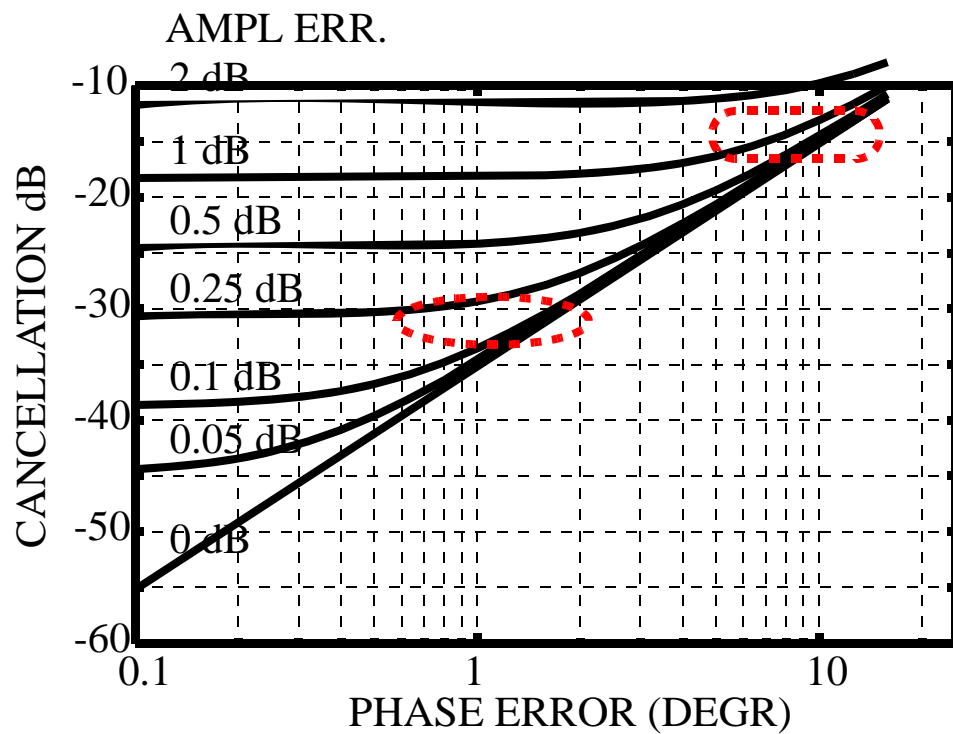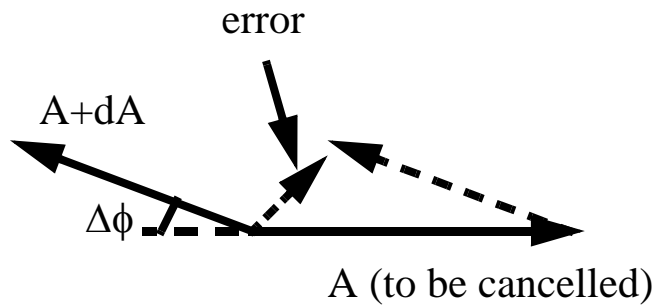

3. VOLTERRA ANALYSIS

Reasoning

- Polynomial modelling makes it easy to track mixing between harmonic bands
- Symbolic analysis grows out of hand -> need numerical tools

Visualization methods


- Vector plots of different contributions
- Different types of analysis

Numerical Volterra analysis / Implementation in APLAC

- 5th-order general Matlab SW NLSIM (Heiskanen)
- VoHB: Combined fitting and analysis on top of harmonic balance of APLAC (Aikio)

Volterra basics

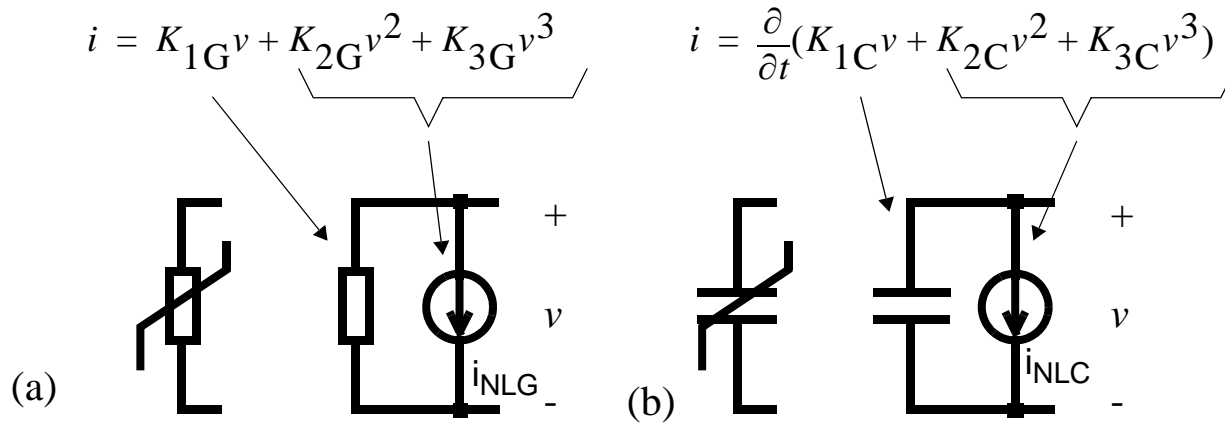Nonlin VCCS -> lin comp. + distortion current source



$$v = v_1 + v_2 + v_3 + \dots$$

$$v^2 = v_1^2 + 2v_1 \cdot v_2 + v_2^2 + \dots$$

Time domain

$$i(t) = K_1 \cdot v + K_2 \cdot v^2 + K_3 \cdot v^3 + \dots$$

⊗ means convolution

Frequency domain

$$I(f) = K_1 \cdot V + K_2 \cdot (V \otimes V) + K_3 \cdot (V \otimes V \otimes V) + \dots$$

$$V = V_1 + V_2 + V_3 + \dots \quad \text{signals = sums of all order signals}$$

$$I(f) = K_1 \cdot V + K_2 \cdot (V \otimes V) + K_3 \cdot (V \otimes V \otimes V) + \dots$$

1st-order

$$= K_1 \cdot V_1$$

2nd-order

$$+ K_2 \cdot (V_1 \otimes V_1) + K_1 \cdot V_2$$



3rd-order

$$+ K_3 \cdot (V_1 \otimes V_1 \otimes V_1) + 2K_2 \cdot (V_1 \otimes V_2) + K_1 \cdot V_3$$



4th-order

$$+ K_4 \cdot (V_1 \otimes V_1 \otimes V_1 \otimes V_1) + 3K_3 \cdot (V_1 \otimes V_1 \otimes V_2) \\ + 2K_2 \cdot (V_1 \otimes V_3) + K_2 \cdot (V_2 \otimes V_2) + K_1 \cdot V_4$$



VISUALIZATION METHODS - IM3 BIAS SWEEP

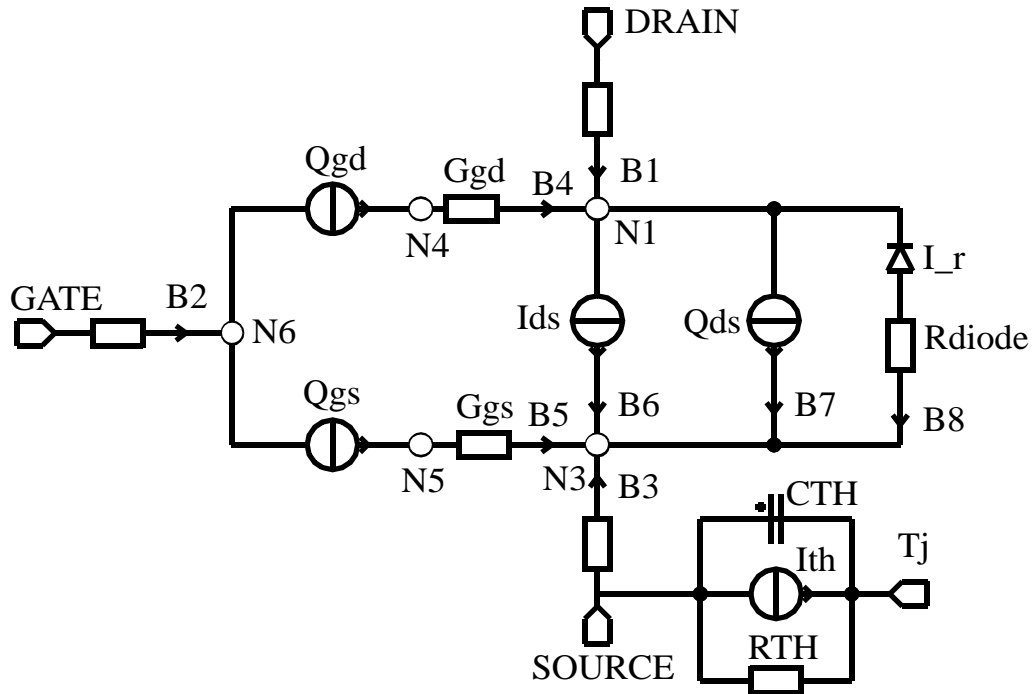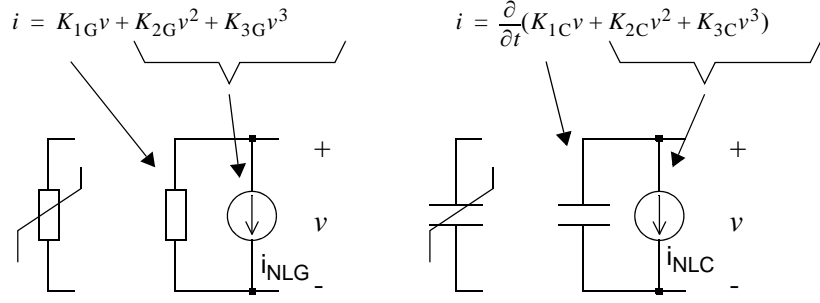

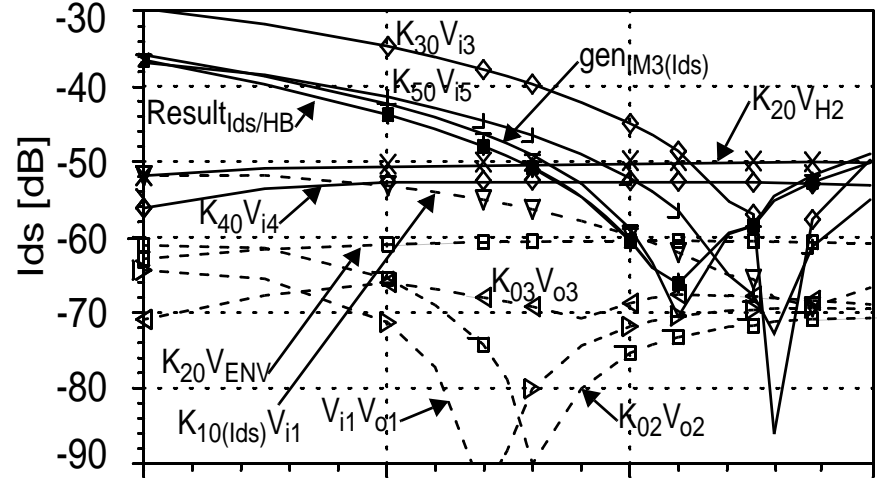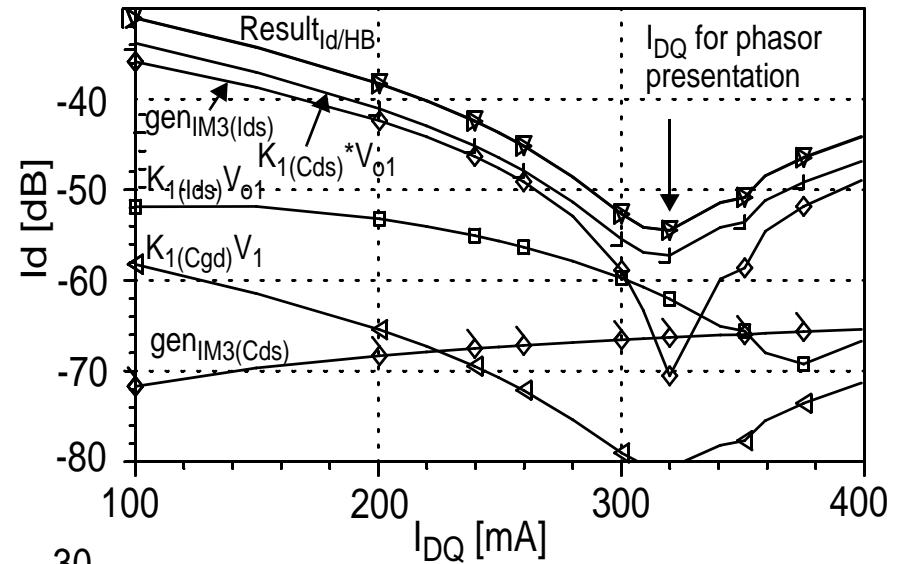Gives a detailed view of what is causing memory effects, for example





IM3 VECTOR SUM AT POINT POWER

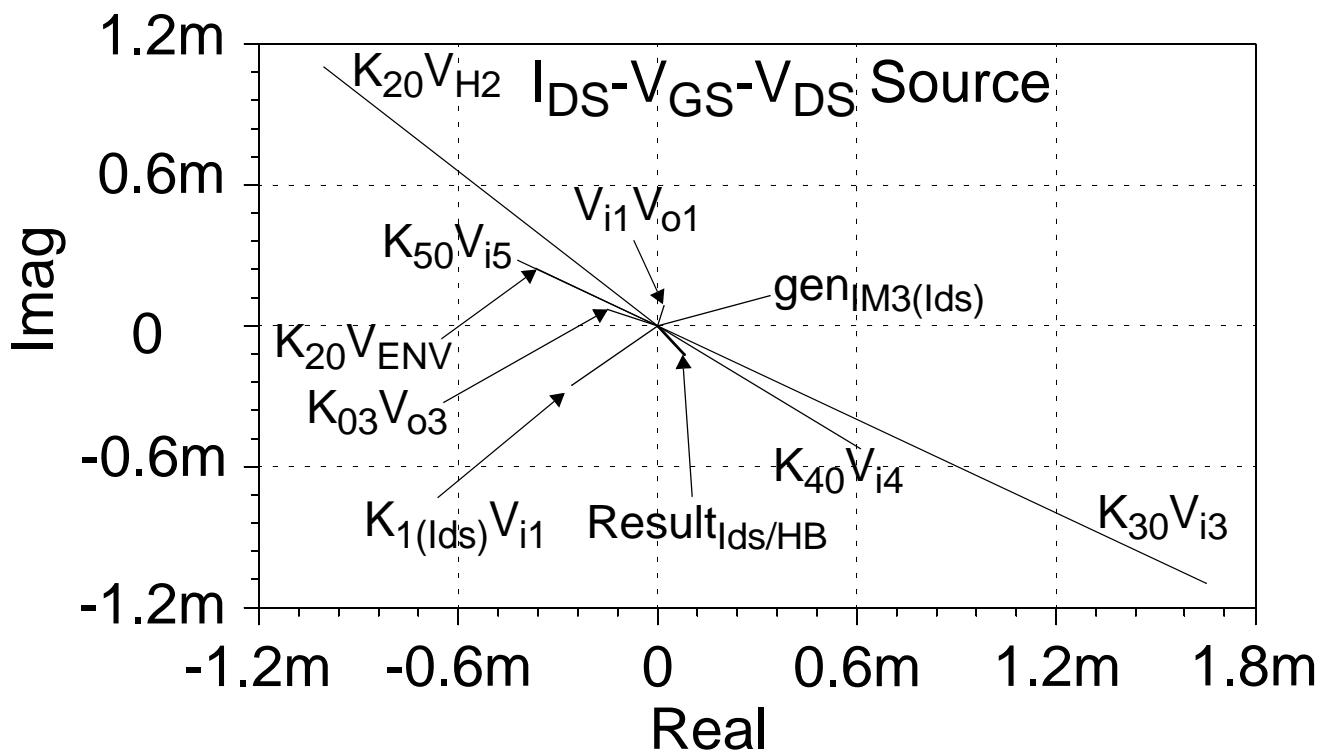
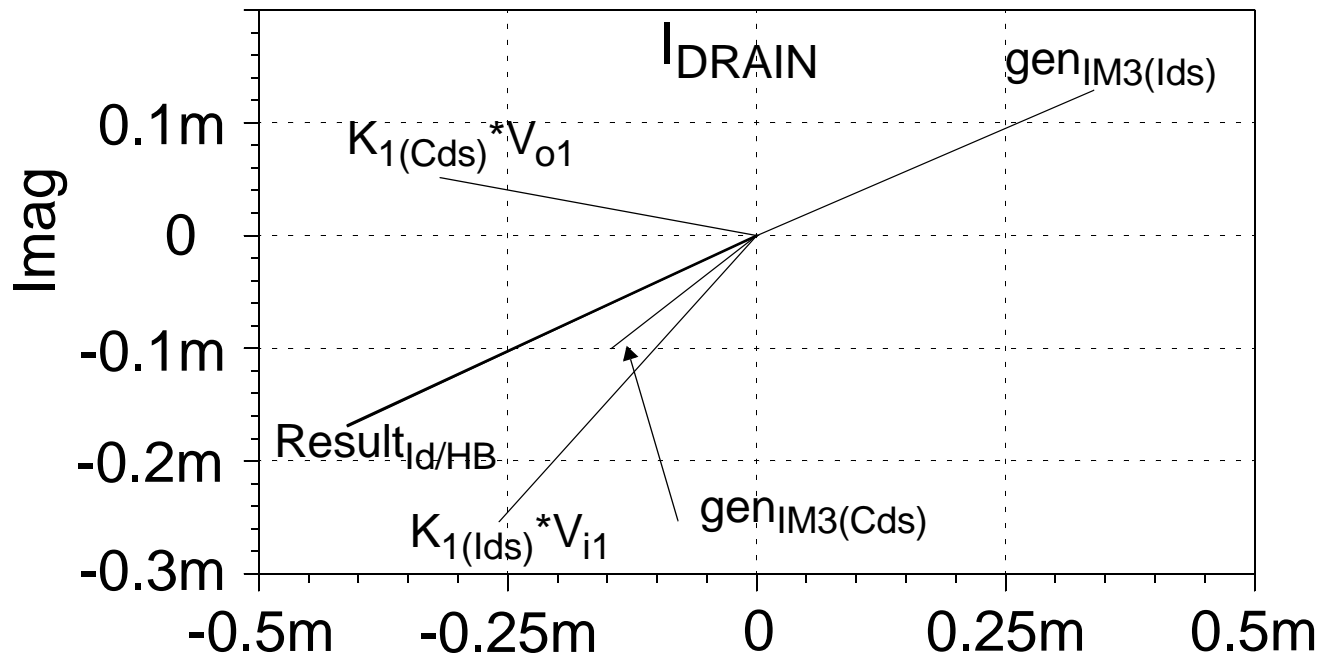


FUNDAMENTAL AMAM/AMPM

- ANALYSIS OF ANY TONE
- AM/AM, AM/PM

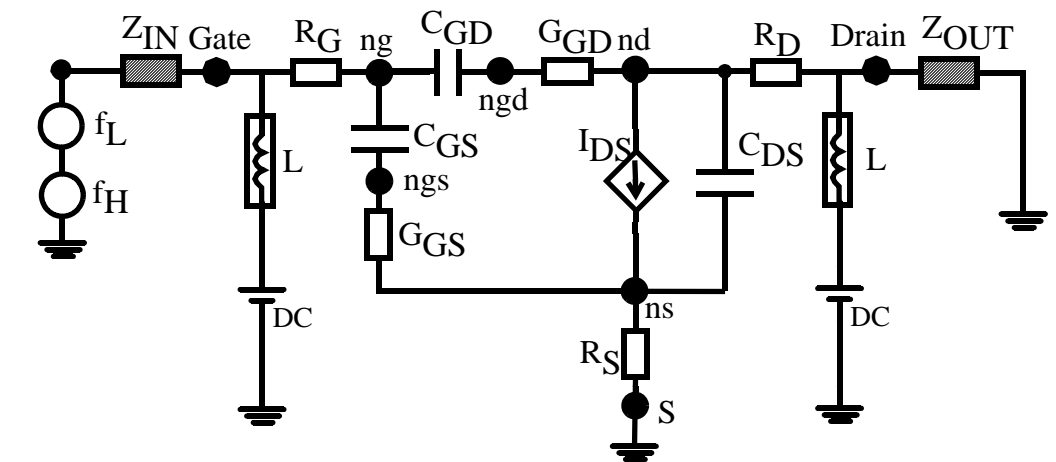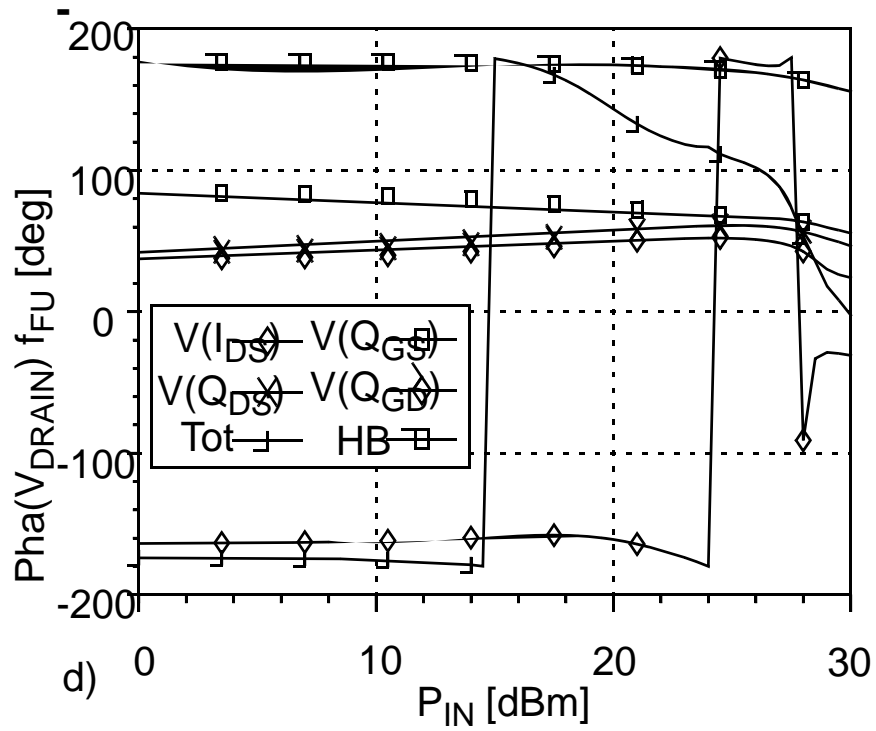


HARMONIC LOAD PULL

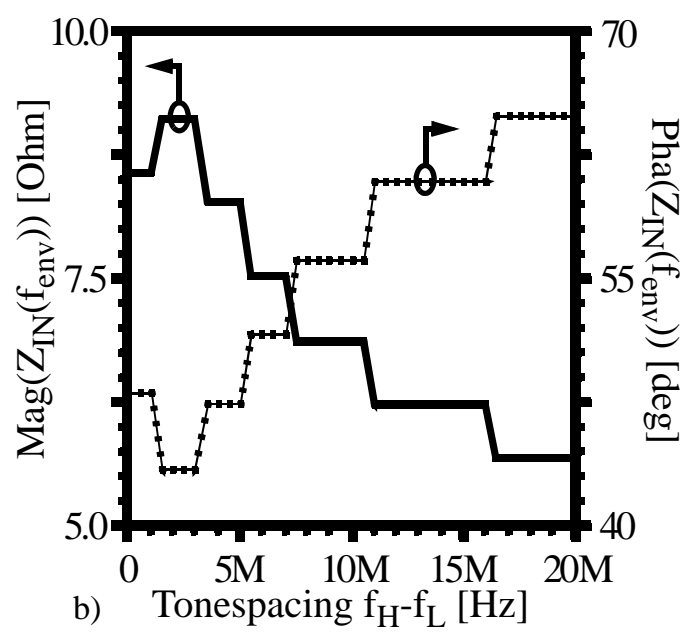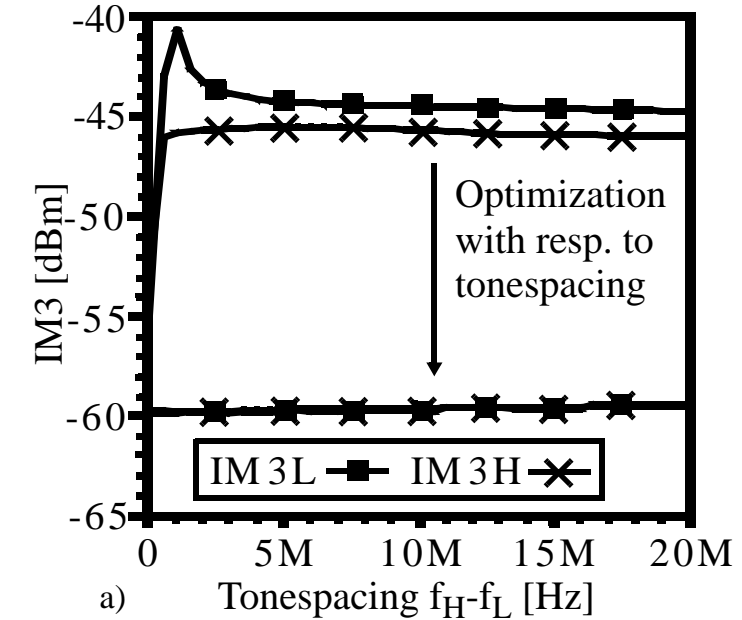

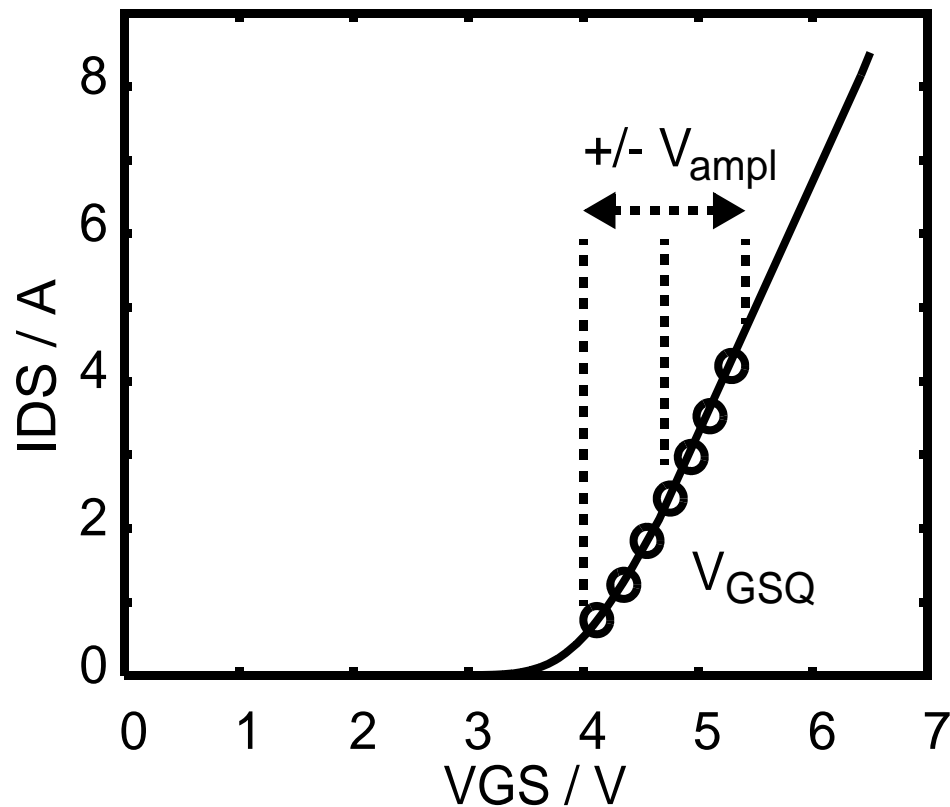4. BUILDING POLYNOMIAL MODELS: I-V Curve Fitting

Pick m data points from the I-V curve
and perform normal LSE fitting
- sensitive to bias & ampl.



$$I_D = K_0 + K_1 v + K_2 v^2 + K_3 v^3$$


$$\begin{matrix} M & & K & & I \end{matrix}$$

$$\begin{bmatrix} 1 & v_1 & v_1^2 & v_1^3 \\ \vdots & \vdots & \vdots & \vdots \\ 1 & v_m & v_m^2 & v_m^3 \end{bmatrix} \cdot \begin{bmatrix} K_0 \\ K_1 \\ K_2 \\ K_3 \end{bmatrix} = \begin{bmatrix} i_1 \\ \vdots \\ i_m \end{bmatrix}$$


$$K = (M^T \cdot M)^{-1} \cdot (M^T \cdot I)$$

Spectral Fitting (core of VoHB)

K1·V

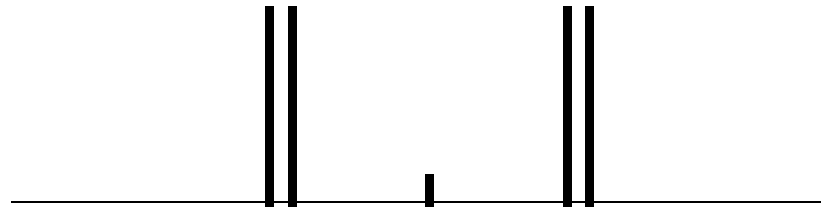


+ K2·(V⊗V)

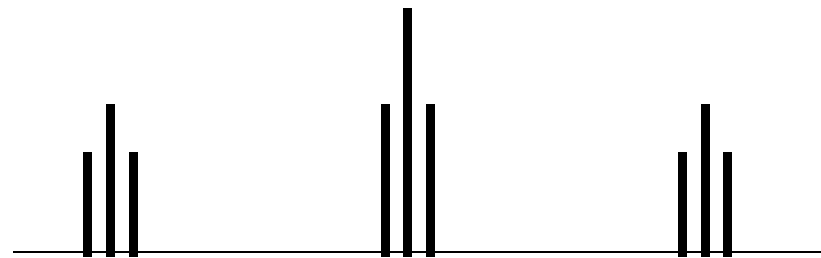

+ K3·(V⊗V⊗V)



= I

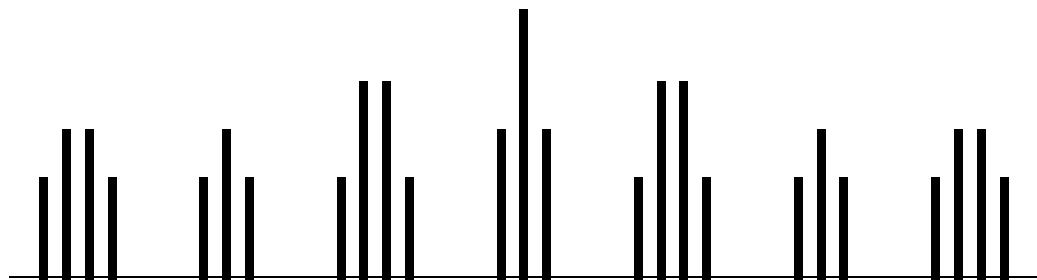

```

pw = [1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 0 0 0 0 0 0 0 0 0 0; ... % enable mask
      0 1 2 3 4 5 0 0 0 0 0 1 2 3 4 2 1 1 1 1 2 3 0 1 0 2 1 0 3 2 1 0; ... % vi
      0 0 0 0 0 0 1 2 3 4 5 1 1 1 1 2 2 3 4 3 2 0 0 1 0 1 2 0 1 2 3]; % vo
      0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 1 1 1 1 1 1 1 1 1 1]; % t

```

```

[icoeff] = fitIds(Idsac,Vgsac,Vdsac,Tac,pw); % fit id-vgs-vds values

```

```





-----
function [coeff] = fitIds(y, x1, x2, t, pow) %%%%%%%%% polynomial fit of Id-Vgs-Vds-T

M = [];
for i=1:length(pow(1,:))
    if pow(1,i) == 1, M = [M (x1.^pow(2,i)).*(x2.^pow(3,i)).*(t.^pow(4,i))]; end
end

if(1>0)
    MMI = (M'*M); fprintf(1,'Condition number: %1.2e \n', cond(MMI));
    coeff = inv(MMI)*(M'*y);
else
    [Q,R] = qr(M); %% QR factorizations
    coeff = R\R'\M'*y);
    est = M*coeff;
    err = y - est;
    coeff = coeff + R\R'\M'*err);
    [mr,nr] = size(R); R = R(1:nr,1:nr);
    MMI = inv(R); MMI = MMI*MMI'; fprintf(1,'Condition number: %1.2e \n', cond(MMI));
end

```

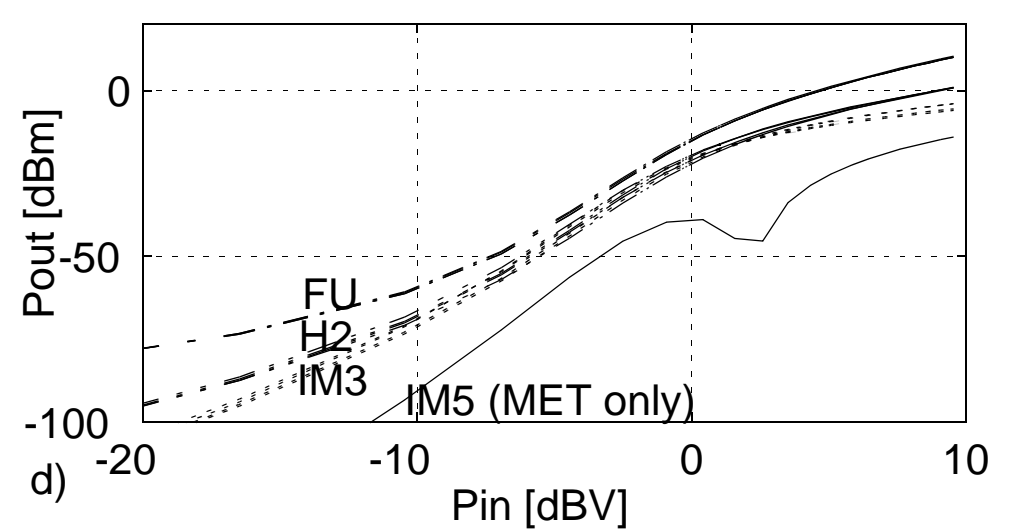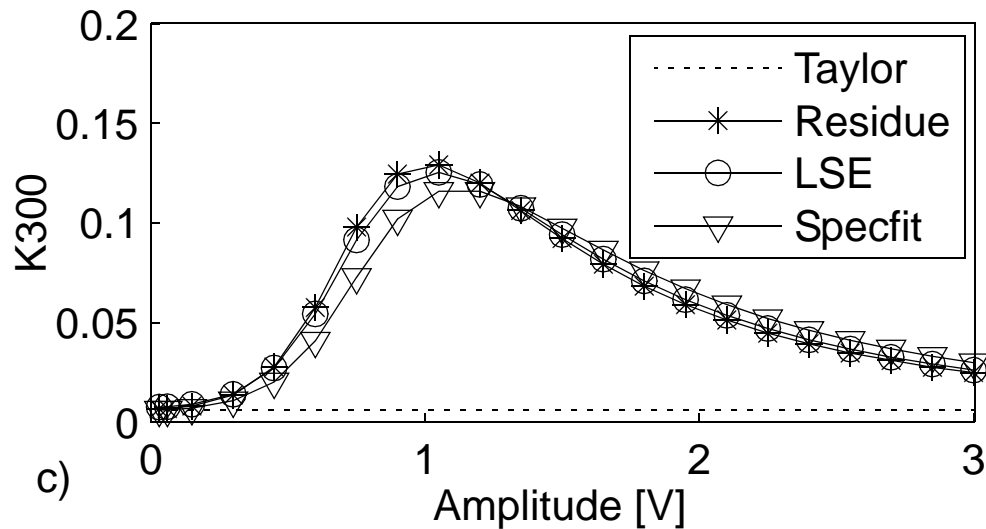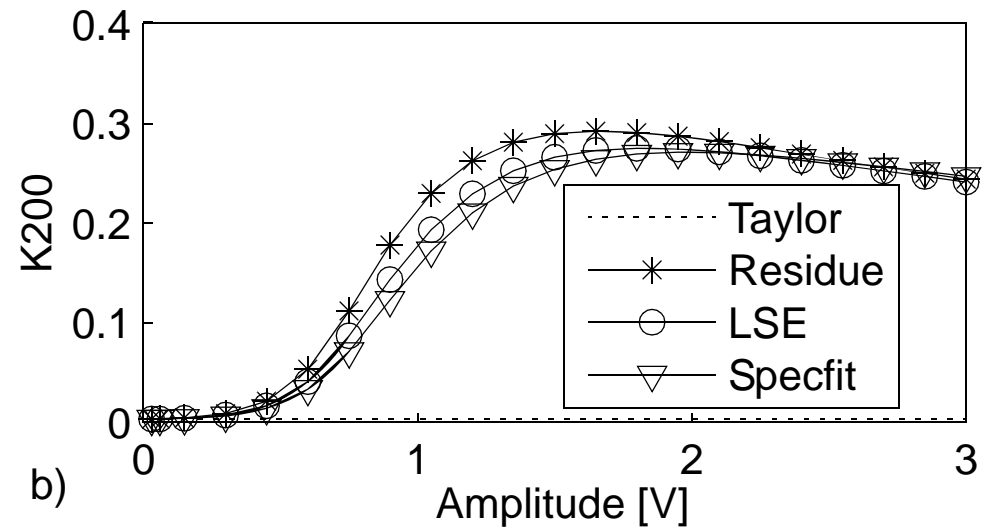
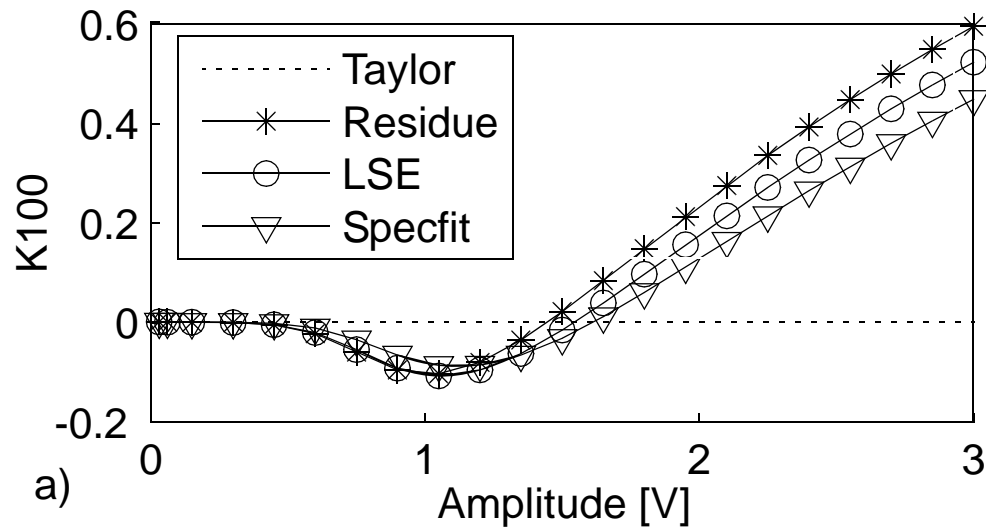
Accuracy of polynomial models - class C LDMOS example



$$i(t) = K_{100} \cdot v + K_{200} \cdot v^2 + K_{300} \cdot v^3$$

Different training signals:
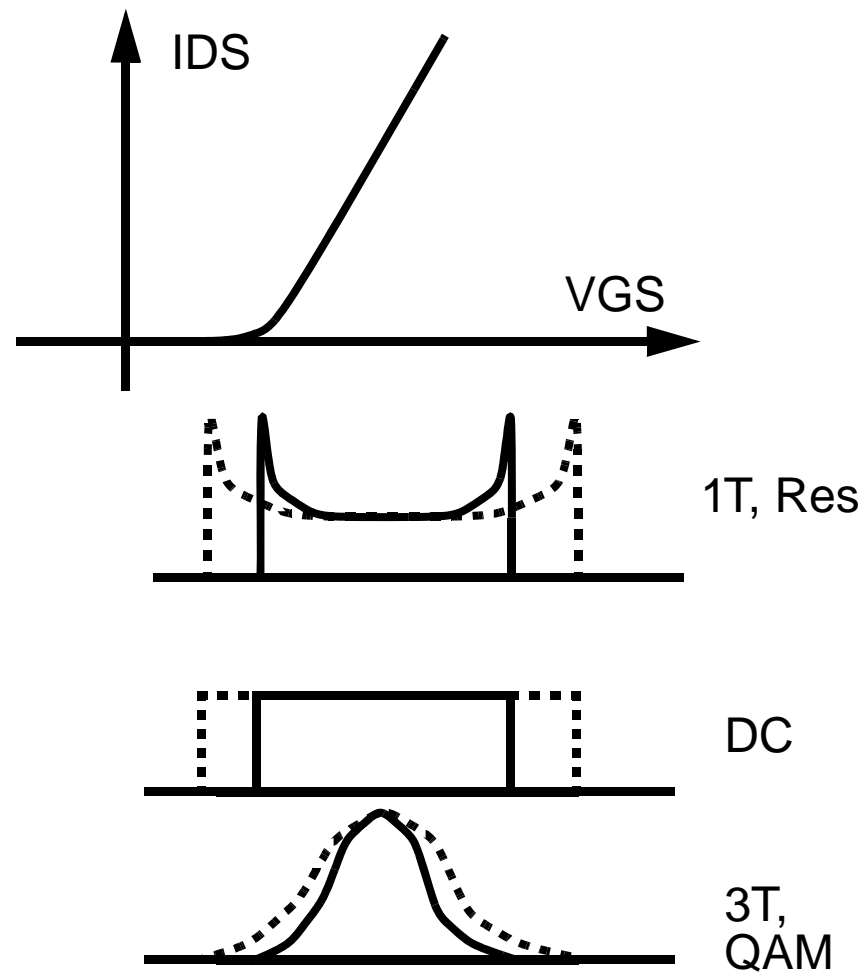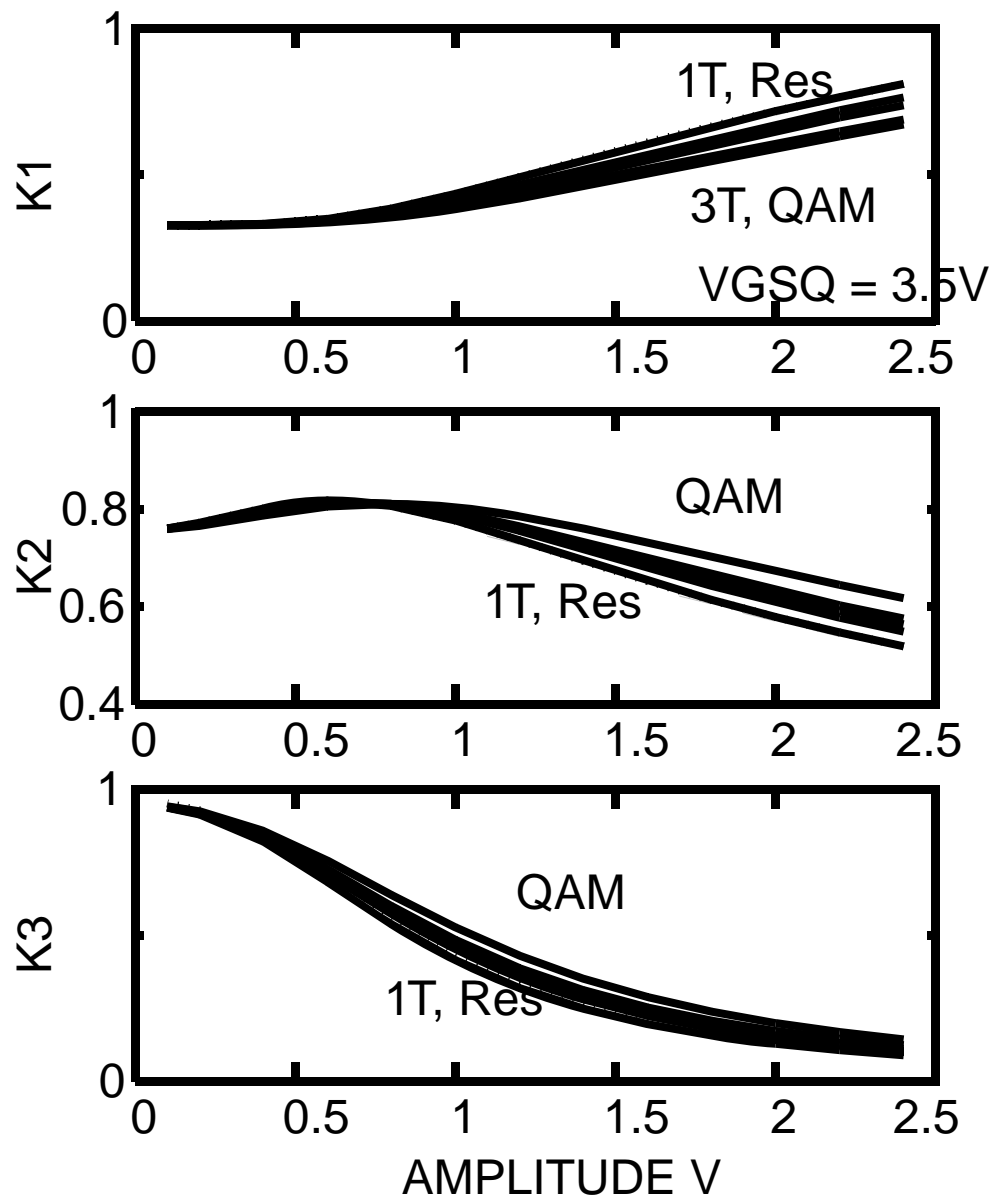
$$I_D = K_0 + K_1 v_{GS} + K_2 v_{GS}^2 + K_3 v_{GS}^3$$



5. IMPLEMENTATIONS OF VOLTERRA ANALYSIS

NLSIM:
$$i(t) = K_1 \cdot v + K_2 \cdot v^2 + K_3 \cdot v^3 + \dots$$

- Solve 1st order voltage spectrums as

$$V_1 = Y^{-1} \cdot I_{in}$$

- Calculate 2nd order current spectrum as

$$I_{NL2} = K_2 \cdot (V_1 \otimes V_1)$$

- Solve 2nd order voltage spectrums as

$$V_2 = Z_T \cdot I_{NL2}$$

- Calculate 3rd order currents as

$$I_{NL3} = K_3 \cdot (V_1 \otimes V_1 \otimes V_1) + 2K_2 \cdot (V_1 \otimes V_2)$$

- Solve 3rd order voltages as

$$V_3 = Z_T \cdot I_{NL3}$$

....


- Store results term-by-term basis

MATLAB SIMULATOR NLSIM

$$v(t) \cdot v(t) \leftrightarrow V(f) \otimes V(f)$$

$$i3 = K3 * \text{conv}(v1, \text{conv}(v1, v1)) + 2 * K2 * \text{conv}(v1, v2)$$

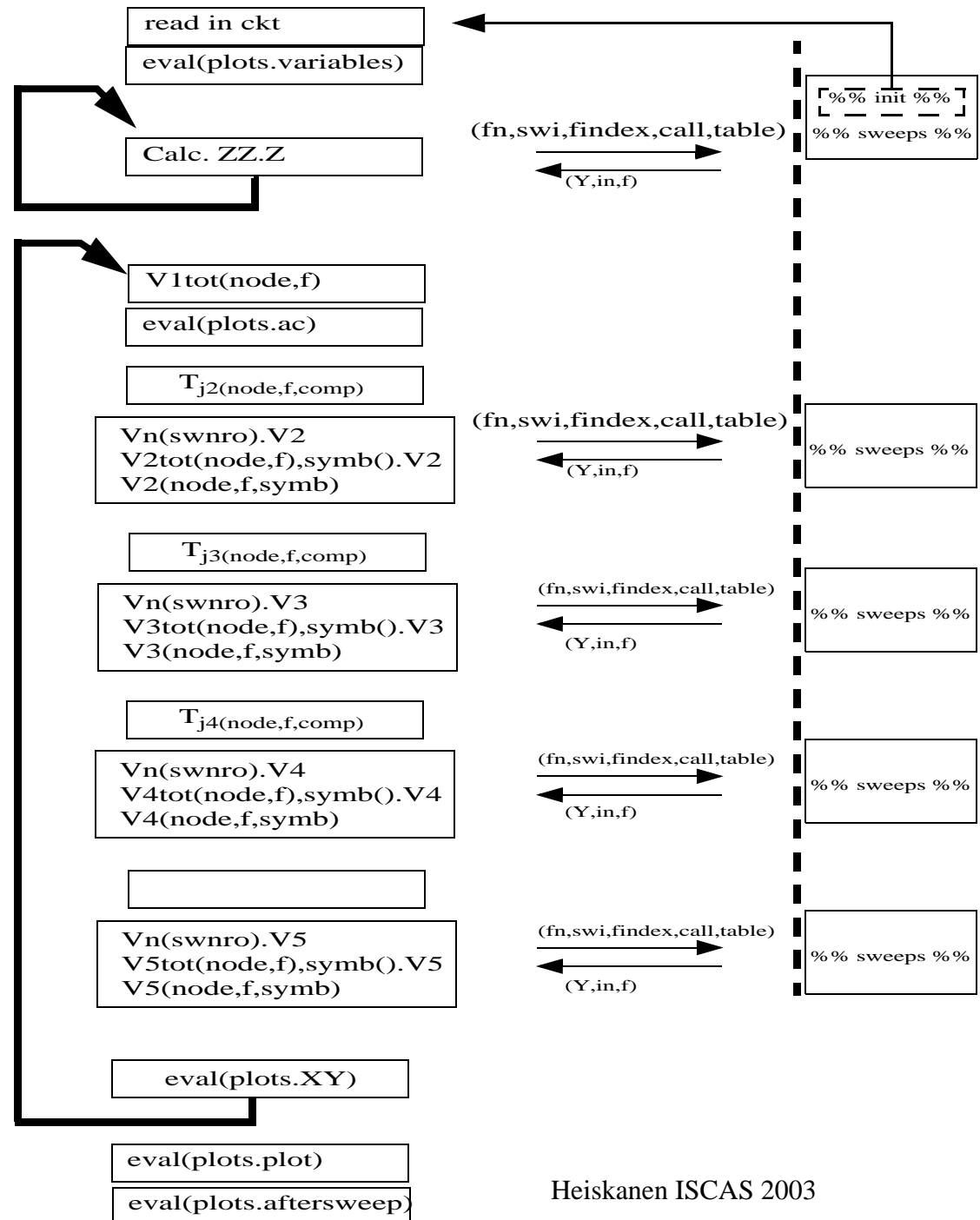- netlist-> y-matrix
- multiport
- envelope injection
- poss. to multitone
- non-optimised implmt.



VoHB: APLAC i code: (now mostly on c lang)

```


Text          pre          (E)
MSub          TLX          (E)
T$xt          Variabl$$s  (E)
OptimM$thod  Tuning       (D)
Circuit Diagram [...]    (E)
Text          d$f         (E)
D$clare      [VECTOR Outp COM...] (E)
Text          DC-Analysis  (E)
Text          Swiippi     (E)
    
```

```

MSub TLX
ER = 2.55
LEVEL = 1
H = 0.7618867m
TAND = 0.0019
T = 35u
    
```

```
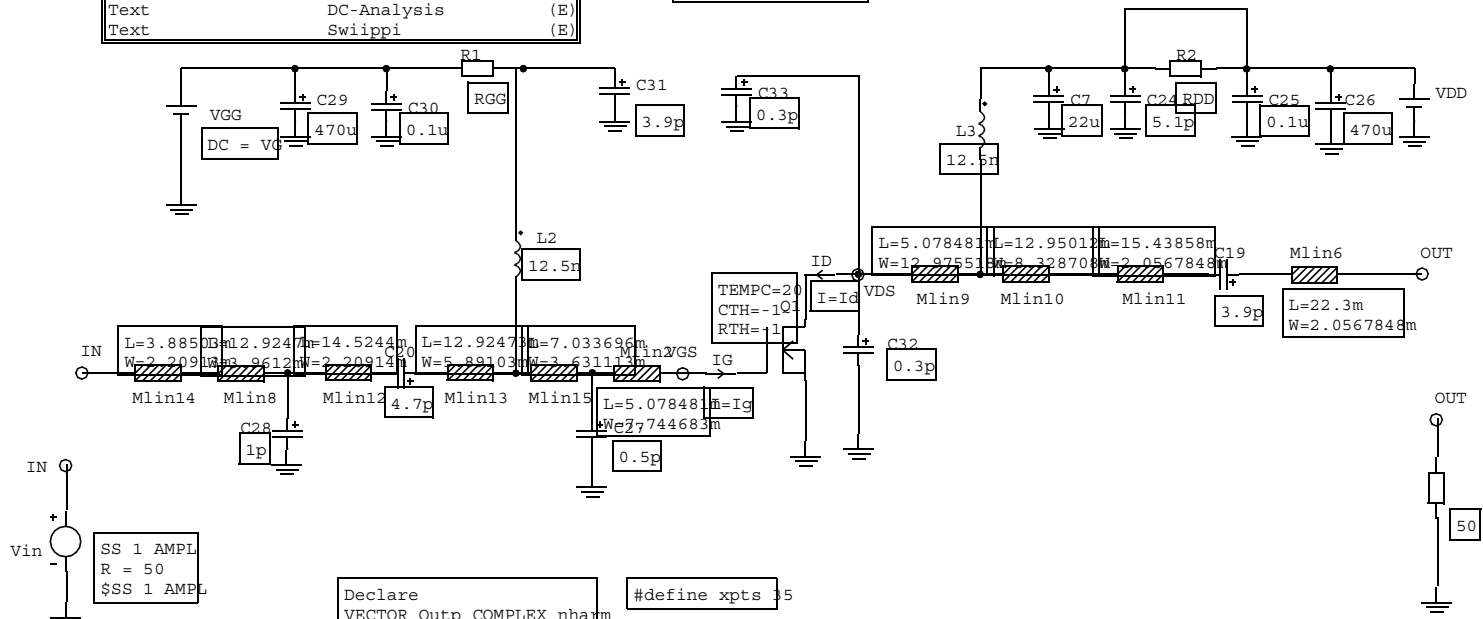
#define nharm 5
Prepare TONE 1 nharm
    
```



```

Declare
VECTOR Outp COMPLEX nharm
VECTOR IOutp COMPLEX nharm
VECTOR Inp COMPLEX nharm
VECTOR Igg COMPLEX nharm
VECTOR Ud COMPLEX nharm
VECTOR POUT REAL xpts
VECTOR ROUT REAL xpts
VECTOR ZOUT COMPLEX xpts
VECTOR ZIN COMPLEX xpts
VECTOR signal REAL xpts
VECTOR F1A REAL xpts
VECTOR F1P REAL xpts
VECTOR F1R REAL xpts
VECTOR F1I REAL xpts
VECTOR I1A REAL xpts
VECTOR H2 REAL xpts
VECTOR H3 REAL xpts
VECTOR H4 REAL xpts
VECTOR H5 REAL xpts
VECTOR gate REAL xpts
VECTOR curr REAL xpts
VECTOR gain REAL xpts
VECTOR vgdg REAL xpts
    
```

```

#define xpts 35
    
```

```

Aplacvar RGG =12.5 opt step 100
Aplacvar RDD = 12.5 opt step 100
Aplacvar VG 3.79 opt st$tp 0.1
Aplacvar VD 28 opt step 0.1
Aplacvar AMPL = 20m
Aplacvar FREQ = 2140Meg
    
```

```

Analyze DC
Sweep "DC-analysis" DC
Print
! S "DC analysis" LF LF
+ S "Vds =" REAL Vdc(VDS) LF
+ S "Vgs =" REAL Vdc(VGS) LF
+ S "Id =" REAL Idc(Id) LF
+ S "Ig =" REAL Idc(Ig) LF LF
+$ S "Tj =" REAL (Vdc(VDS)*Idc(Id)*Rthjs + Ta) LF
$+PUBLICS
EndSweep
    
```

```

Aplacvar k
For 1 1 xpts
call AMPL = 10**((1-1)/22)

Sw$Sp "sika" SS
+ FO=FREQ
+ WINDOW 0
+ X "FREQ" "Hz" 0 (nharm+1)*FREQ
+ Y "sika" "dB" -60 20

Call Outp=Spectrum(out)

EndSweep

call F1A[1-1]=mag(Outp[1])
call F1P[1-1]=pha(Outp[1])
call H3[1-1]=mag(Outp[3])

call signal[1-1]=AMPL
call gain[1-1] = F1A[1-1]/AMPL

EndFor

Sweep "Power sweep"
+ LOOP xpts APLACVAR k LIN 0 1
+ WINDOW 1
+ X "Uin" "V" 0 0.5
+ Y "Uout" "V" 0 1
+ WINDOW 2
+ X "Uin" "V" 0 0.5
+ Y "Gain" "V" 0 5

Display Window 1
+ VECTOR xpts
+ XY "Uout" signal F1A Mark$r 1
+ XY "H3" signal H3 Mark$r 2
+ XY2 "AM/PM" signal F1P Mark$r 3


Display Window 2
+ VECTOR xpts
+ X "Uin" signal
+ Y "Uout" gain Mark$r 1

EndSweep
    
```


3000 lines
of code ...

Fitting + Volterra on top of Harmonic balance

Simulation procedure:

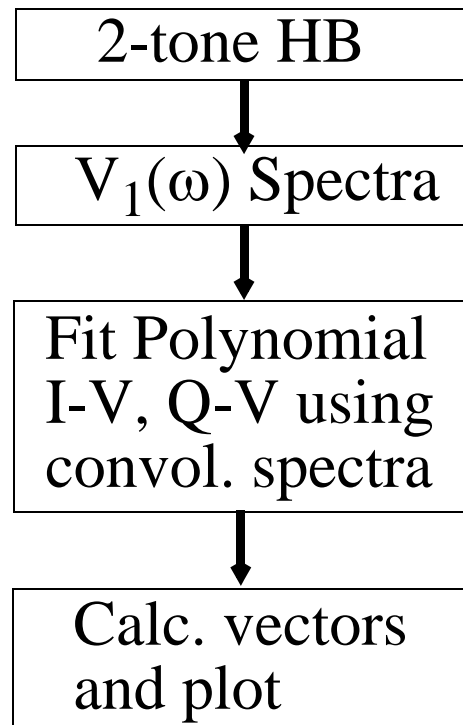

Intrinsic MET model:

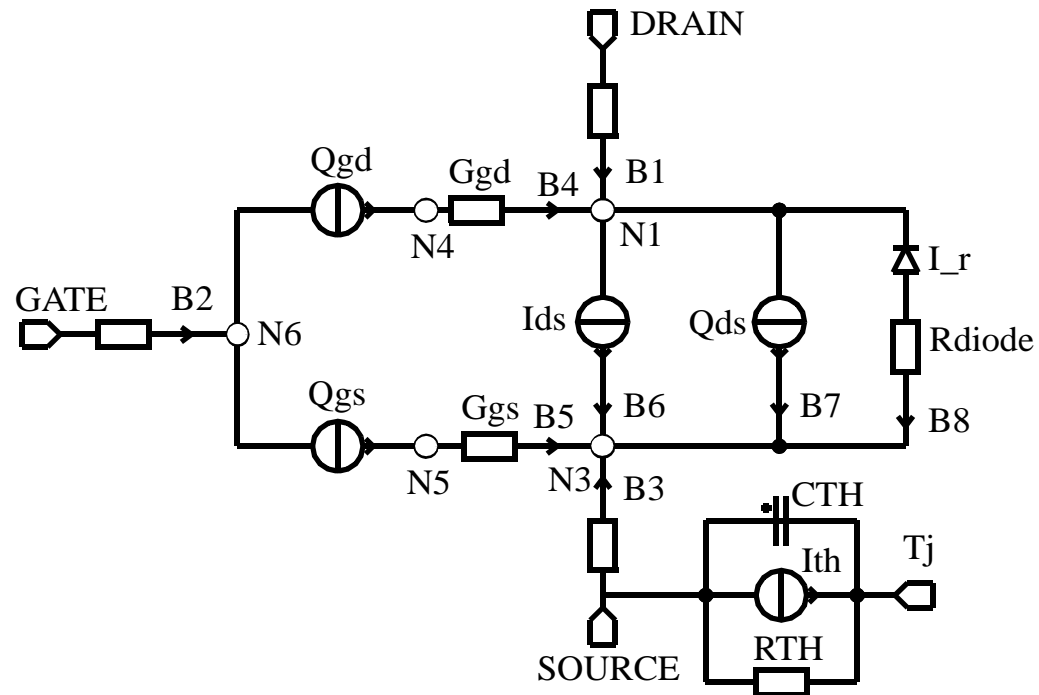

J. Aikio, T. Rahkonen:

IEEE Trans. on MTT, vol. 53 , no. 10 , October 2005, pp.

Frequency domain fitting + contribution analysis

$$v_1(t) \cdot v_2(t) \leftrightarrow V_1(f) \otimes V_2(f) ,$$

$$i(t) = K_0 + K_{10} \cdot v(t) + K_{20} \cdot v(t)^2 + K_{30} \cdot v^3(t)$$

$$\begin{bmatrix} v_1(f) & v_2(f) & v_3(f) \end{bmatrix} \cdot \begin{bmatrix} K_{10} \\ K_{20} \\ K_{30} \end{bmatrix} = \begin{bmatrix} I_{ds}(f) \end{bmatrix} .$$

Solve $\mathbf{K} = (\mathbf{V}^T \mathbf{V})^{-1} (\mathbf{V}^T \mathbf{I})$

Use \mathbf{K} to calculate IM3 current as a sum of contributions

$$\begin{aligned} I_{DS}(f_{IM3}) = & K_{10} \cdot V_{i1}(f_{IM3}) + 2K_{20} \cdot V_{ENV}(f_{IM3}) + 2K_{20} \cdot V_{H2}(f_{IM3}) \\ & + K_{30} \cdot V_{i3}(f_{IM3}) + K_{01} \cdot V_{o1}(f_{IM3}) + K_{02} V_{o2}(f_{IM3}) \\ & + K_{03} \cdot V_{o3}(f_{IM3}) + K_{11} \cdot V_{i1} V_{o1}(f_{IM3}) \\ & + K_{21} \cdot V_{i2} V_{o1}(f_{IM3}) + K_{12} \cdot V_{i1} V_{o2}(f_{IM3}) \end{aligned}$$

6. GOING ON

Polynomial fitting + Volterra into Aplac

- c implementation using AIF interface
- arbitrary number of VCCS -> multidevice analysis
- new convolution algorithm supports multitone analysis

Extensions

- Harmonic load pull using Volterra (i implementation ready)
- Yet new ways of finding polynomial coefficients

To be done in the next episode

- Complex transmitter structures: Feedforward, Doherty amplifier, ET, ...
- Usability in large signal stability analysis ?